

PIEZOELECTRIC MATERIALS

PIEZOELECTRICITY - property of some crystalline solids to generate electrical charges on their surfaces following a mechanical strain inducing a deformation

opposite polarities on opposite sides determined by measuring voltage btw electrodes on surfaces

DIRECT
PIEZOELECTRIC
EFFECT
vs

mechanical stress (forces)

elastic material

mechanical deformation

electrical charge

instruments (accel./ force/ pressure)

INVERSE
PIEZOELECTRIC
EFFECT

external electric field


polarization (electrical charge) dielectric material

mechanical deformation

US systems (mech. waves)

energy conversion (direction sensitive)

NON PIEZOELECTRIC MATERIALS

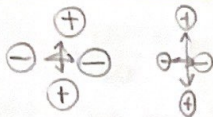


• symmetric charge distribution (average location of \ominus and \oplus charges matches)
→ no electrical response to mechanical force

PIEZOELECTRIC MATERIALS

crystalline solid \equiv repetition of structural unit (UNIT/ELEMENTARY CELLS) of simple geometrical shape

• asymmetric charge distribution (average locations do not match)

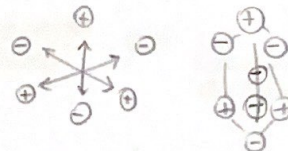[unperturbed condition → average location matches]



deformation determines DIPOLE


opposite polarities on the 2 sides

- NATURAL CRYSTALS (quartz)
- SYNTHETIC CRYSTALS
- POLARIZED FERROELECTRIC CERAMICS (ultrasound transducer)

or \vec{E} applied → charge separation → deform. of the structure

Behavior depending on material cut of slab wrt crystalline solid

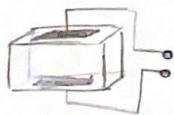- THICKNESS EXPANSION
- TRANSVERSE EXPANSION
- THICKNESS SHEAR
- FACE SHEAR



METAL ELECTRODES placed over selected surfaces of PE.

+ LEAD WIRES bringing in or leading out electrical charges

~ capacitor's plates with dielectric material within it

MECHANICAL INPUT (mechanical deformations)

→ charge Q is generated

→ voltage drop

$$V = \frac{Q}{C_s}$$

C_s : capacitance of p.e

PIEZOELECTRIC DISPLACEMENT SENSORS

AIM: measure F , accelerations and pressure


DISPLACEMENT x
due to a force
(\equiv thickness a)

charge Q
is generated

voltage
drop V
across the 2 faces

$$Q = K_d x$$
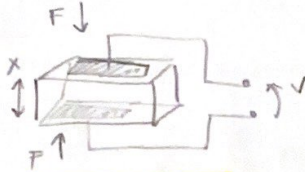
$$V = \frac{Q}{C_s} = \frac{K_d x}{C_s}$$



K_d [C/m] constant characteristic of the p. sensor depending on material

EQUIVALENT ELECTRICAL CIRCUIT: charge generator // capacitance


of electrical behavior of charge sensor

$i(t)$

charge & displacement

C_s

charge converted into voltage

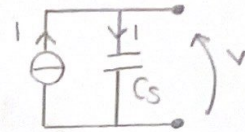

$$i(t) = \frac{dQ(t)}{dt} = K_d \frac{dx(t)}{dt}$$

converted into current generator

current entirely flows across C_s $i(t) = C_s \frac{dV(t)}{dt}$

$$i(t) = C_s \frac{dV(t)}{dt} = K_d \frac{dx(t)}{dt}$$

$$\frac{dV(t)}{dt} = \frac{K_d}{C_s} \frac{dx(t)}{dt}$$

$$V(t) = \frac{K_d}{C_s} \int dx(t) \rightarrow V(t) = \frac{K_d}{C_s} x(t)$$

Voltage across 2 faces \propto displacement of the 2 faces

INPUT: step (dynamic performance) } perfect sensor
OUTPUT perfectly reproduces the step


BUT not complete description

Piezoelectric element is not a perfect dielectric material with ∞ resistivity (= no conductivity)

(high but not ∞)


[G Ω - hundreds G Ω]

output tends to decay over time

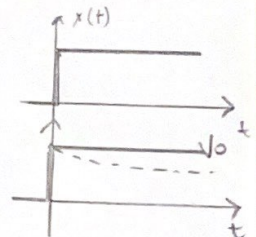

LEAKAGE RESISTANCE R_s // C_s // current generator

QUASI-STATIC RESPONSE

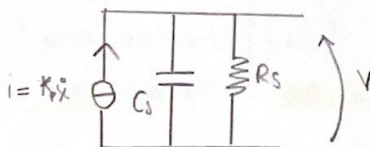


VOLTAGE AMPLIFIER

displacement sensor connected to **CONDITIONING BLOCK** through **cables** (connecting c)

R_{in} input resistance $\ll R_s$
(impedance matching: R_{in} high to not lose energy)

introduction of capacitance


Cables parasitic capacitance

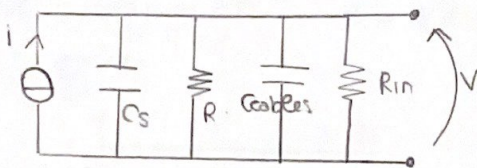

$$R = R_{in} // R_s$$

$$C = C_s // C_{cables} = C_{in} + C_{cables}$$

overall circuit

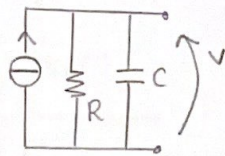

$$Z(s) = \frac{1}{sC + \frac{1}{R}} = \frac{R}{1 + sRC}$$

$$V(s) = \frac{R}{1 + sRC} i(s)$$

$$i(t) = k_p \dot{x}(t)$$

$$i(s) = k_p s X(s)$$

$$V(s) = \frac{R k_p s}{1 + sRC} X(s)$$

$$G(s) = \frac{V(s)}{X(s)} = \frac{k_p R s}{1 + sRC} \cdot \frac{C}{C} =$$

$$= \frac{k_p}{C} \frac{sRC}{1 + sRC}$$

where $\tau = RC$ TIME CONSTANT

$$|K| = \frac{k_p}{C} \text{ dB}$$

+20 dB/dec

1st order HP filter

$$K = \frac{k_p}{C} \text{ sensitivity / passband gain}$$

$$V_u(s) = \left(\frac{k_p}{C} \right) \frac{s\tau}{1 + s\tau} X(s)$$

$$(1 + s\tau) V_u(s) = k s \tau X(s)$$

$$V_u + s\tau V_u(s) = k s \tau X(s) \longrightarrow V_u(t) + \tau \frac{dV_u(t)}{dt} = k \tau \frac{dx(t)}{dt}$$

$$\tau \frac{dV_u(t)}{dt} + V_u(t) = k \tau \frac{dx(t)}{dt}$$

non homogeneous 1st order diff. eq

$$x(t), v(t) = 0 [t < 0]$$

$x(t)$ = forcing action

STEP INPUT: $x(t) = L$ for $0 < t < T \Rightarrow \frac{dx}{dt} = 0$ (sudden change of x btw 0^- and 0^+)

$$\tau \frac{dV_u(t)}{dt} + V_u(t) = 0 \text{ homogeneous 1st order diff. eq}$$

$$IC: V_u(0^+) = KL$$

↓
HIGH-PASS BEHAVIOR
⇒ sudden change of the output

$$V_u(t) = A e^{-t/\tau}$$


$$A = KL$$

$$V_u(t) = KL e^{-t/\tau} \quad 0 < t < T \text{ exponential decrease from } VL \text{ to zero}$$

$t = T^-$ $x(T^-) = L$ } sudden change $\rightarrow V_u$: sudden change of $-kL$
 $t = T^+$ $x(T^+) = 0$ of L

IC: $V(T^+) = kLe^{-T/\tau} - kL$

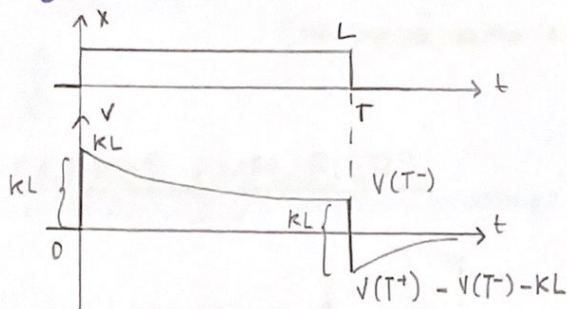$V_u(t) = Be^{-t/\tau}$ $Be^{-T/\tau} = kLe^{-T/\tau} - kL \rightarrow V_u(t) = (kLe^{-T/\tau} - kL)e^{-\frac{t-T}{\tau}}$
 NB: x constant = 0 for $t > 0$ $B = e^{\frac{T}{\tau}} (kLe^{-T/\tau} - kL)$ exponential increase from $V(T^+)$ to zero
 $\frac{dx}{dt} = 0$



Gain: faithful reproduction of the input

$G \uparrow \equiv \omega_c \downarrow$ improving response at low freq

$\hookrightarrow C \uparrow, R \uparrow$, both \uparrow

INCREASE C capacitance C_{par} inserted in parallel

$C' = C + C_{par}$
 $= C_s + C_{cables} + C_{par}$

INCREASE R $R = \frac{R_{in}R_s}{R_{in}+R_s} \approx R_{in}$ since $R_s \gg R_{in}$


$R_{in} \uparrow$ changing amplifier

$G' = RC'$

$k' = \frac{k_p}{C'}$ } NB. $k' \downarrow$ if $C \uparrow$
 loss in sensitivity

R_{ser} inserted in series to R_{in}

$R_s \approx \infty$ open circuit

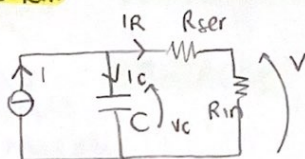

$K \frac{dx(t)}{dt} = C \frac{dV_c(t)}{dt} + \frac{V(t)}{R_{in}}$

$C(1 + \frac{R_{ser}}{R_{in}}) \frac{dV(t)}{dt} + \frac{1}{R_{in}} V(t) = Kq \frac{dx(t)}{dt}$

$\frac{C}{R_{in}} (R_{ser} + R_{in}) s V(s) + \frac{V(s)}{R_{in}} = Kq s X(s)$


$Kq s X(s) = \frac{V(s)}{R_{in}} (1 + sC(R_{ser} + R_{in}))$

$\frac{V(s)}{X(s)} = \frac{sKqR_{in}}{1 + sC(R_{in} + R_{ser})} \cdot \frac{C}{C} = \frac{Kq \cdot sR_{in}C}{1 + sC(R_{in} + R_{ser})} \cdot \frac{(R_{in} + R_{ser})}{(R_{in} + R_{ser})}$
 $= \frac{K}{C} \frac{R_{in}}{R_{ser} + R_{in}} \frac{sC(R_{in} + R_{ser})}{(1 + sC(R_{in} + R_{ser}))}$

$i_c(t) = C \frac{dV_c(t)}{dt}$

$i_R(t) = \frac{V(t)}{R_{in}}$

$i(t) = Kq \frac{dx(t)}{dt}$

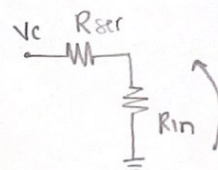

voltage divider $V = \frac{R_{in}}{R_{in} + R_{ser}} V_c$

$V_c = V \frac{R_{in} + R_{ser}}{R_{in}} = V(1 + \frac{R_{ser}}{R_{in}})$

$$\Rightarrow G(s) = \frac{k_q}{C} \frac{R_{in}}{R_{in} + R_{ser}} \frac{sC(R_{in} + R_{ser})}{1 + sC(R_{in} + R_{ser})}$$

$$G'' = (R_{in} + R_{ser})C$$

$$K'' = \frac{k_q}{C} \frac{R_{in}}{R_{in} + R_{ser}}$$

loss in sensitivity

LIMITATIONS

1st order HP filter

(sensor + cables + amplifier)

\uparrow enlarging passband zone to lower freq BUT UNABLE to respond to STATIC / LOW-FREQ PHENOMENA

sensitivity / G always depend on C , including C_{cables} (NR longer cables $\downarrow K$) parasitic parameters




CHARGE AMPLIFIERS

some advantages compared to voltage amplifier

V_u output of charge amplifier due to C_f in feedback branch who determines the dynamics of the system

$$C = C_s + C_{cables}$$

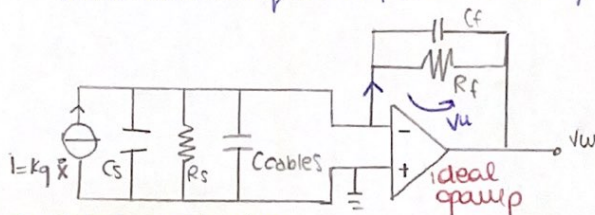

charge generated by piezoelectric element totally transferred on C_f and discharged through R_f

$$V^+ = V^- = 0 \quad \text{rule 1} \\ V_d = 0$$

$\rightarrow i = k_q \times \text{flow only across feedback branch}$ } why called charge amplifier
 $I_C = I_R = 0$

$$I_f(s) = \frac{1}{sC_f + 1} = \frac{R_f}{1 + sC_f R_f}$$

$$V_u(s) = -I(s) \frac{R_f}{1 + sC_f R_f} = -k_q \frac{s R_f}{1 + sC_f R_f} X(s) \left[\frac{C_f}{C_f} \right] = -\frac{k_q}{C_f} \frac{s R_f C_f}{1 + s R_f C_f} X(s)$$

$$I(s) = k_q s X(s)$$

$$\Rightarrow G(s) = -\frac{k_q}{C_f} \frac{s C_f R_f}{1 + s C_f R_f}$$

$$k = -\frac{k_q}{C_f}$$

sensitivity (high-freq gain)

$$G = R_f C_f$$

time constant

constant < 0 \rightarrow zero in origin + real pole
same transfer function \downarrow

(NB) HIGH FREQ RESPONSE is not modified (with inability to respond to static/low freq phenomena)


BUT k/G do not depend on C_{cables} (only on design parameters)

We small if $G \uparrow$ $\left\{ \begin{array}{l} R_f \uparrow \\ C_f \uparrow \end{array} \right\}$ or both
(enlarge low freq. passband zone)

but $C_f \uparrow \equiv k \downarrow \Rightarrow$ more convenient $R_f \uparrow$ to G

DC PARAMETERS

$C =$ open circuits

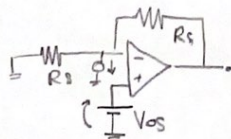

$$V_{u,offset} = V_{os} \left(1 + \frac{R_f}{R_s} \right) + I^- R_f$$

$R_f \uparrow \Rightarrow \uparrow$ effect of I^- bias current

\uparrow NOISE